

CLOCK DIVIDER USING COUNTER

Verilog code:

```
module clock_div (  
    input wire clk,  
    input wire rst,  
    output reg divided_clk  
);  
  
    reg [2:0] counter;  
  
    always @(posedge clk or posedge rst) begin  
        if (rst) begin  
            counter <= 3'b000;  
            divided_clk <= 1'b0;  
        end else begin  
            if (counter == 3'b111) begin  
                counter <= 3'b000;  
                divided_clk <= ~divided_clk;  
            end else begin  
                counter <= counter + 1;  
            end  
        end  
    end  
  
endmodule
```

TESTBENCH:

```
module clock_div_tb
```

```
    reg clk;
```

```
    reg rst;
```

```
    wire divided_clk;
```

```
    clock_div uut (
```

```
        .clk(clk),
```

```
        .rst(rst),
```

```
        .divided_clk(divided_clk)
```

```
    );
```

```
    initial begin
```

```
        clk = 0;
```

```
        forever #5 clk = ~clk;
```

```
    end
```

```
    initial begin
```

```
        rst = 1;
```

```
        #15;
```

```
        rst = 0;
```

```
    #250
```

```
    $finish;
```

```
    end
```

```
    initial begin
```

```
        $display("Time\tclk\trst\tdivided_clk");
```

```
        $monitor("%0dns\t%b\t%b\t%b", $time, clk, rst, divided_clk);
```

```
    end endmodule
```

BLOCK DIAGRAM:

Counter as clock divider

 


Figure 1: Block diagram

Figure 1 BLOCK DIAGRAM

Figure 1 BLOCK DIAGRAM

Truth table:

Clock cycle	Q1	Q0
0	0	0
1	0	1
2	1	0
3	1	1
4	0	0
5	0	1
6	1	0
7	1	1

Figure 2 TRUTTH TABLE

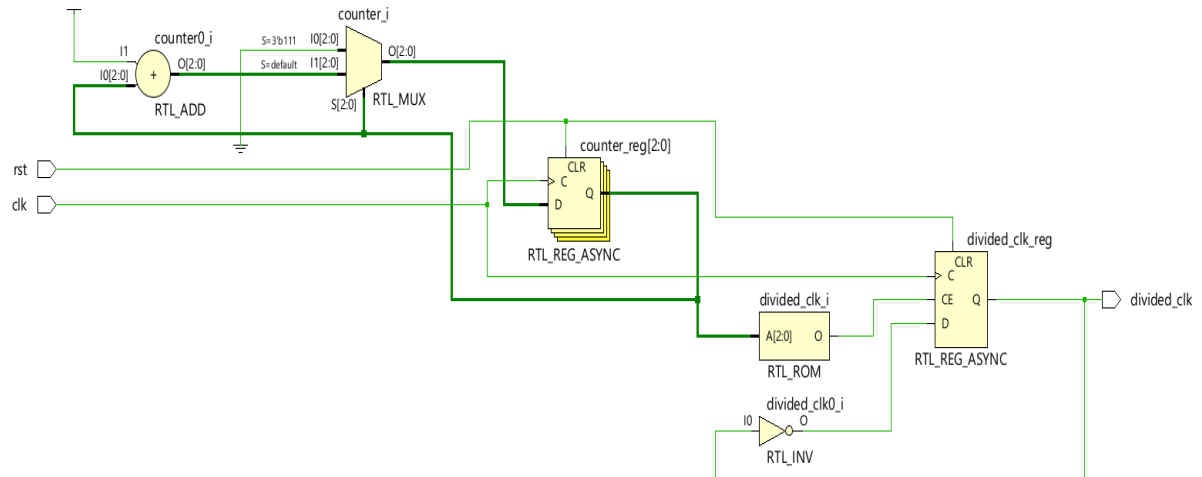


Figure 3 RTL SCHEMATIC

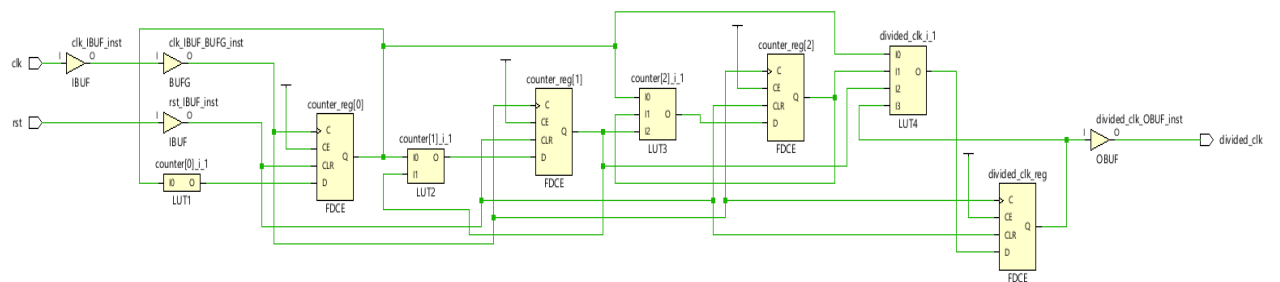


Figure 4 synthesis schematic

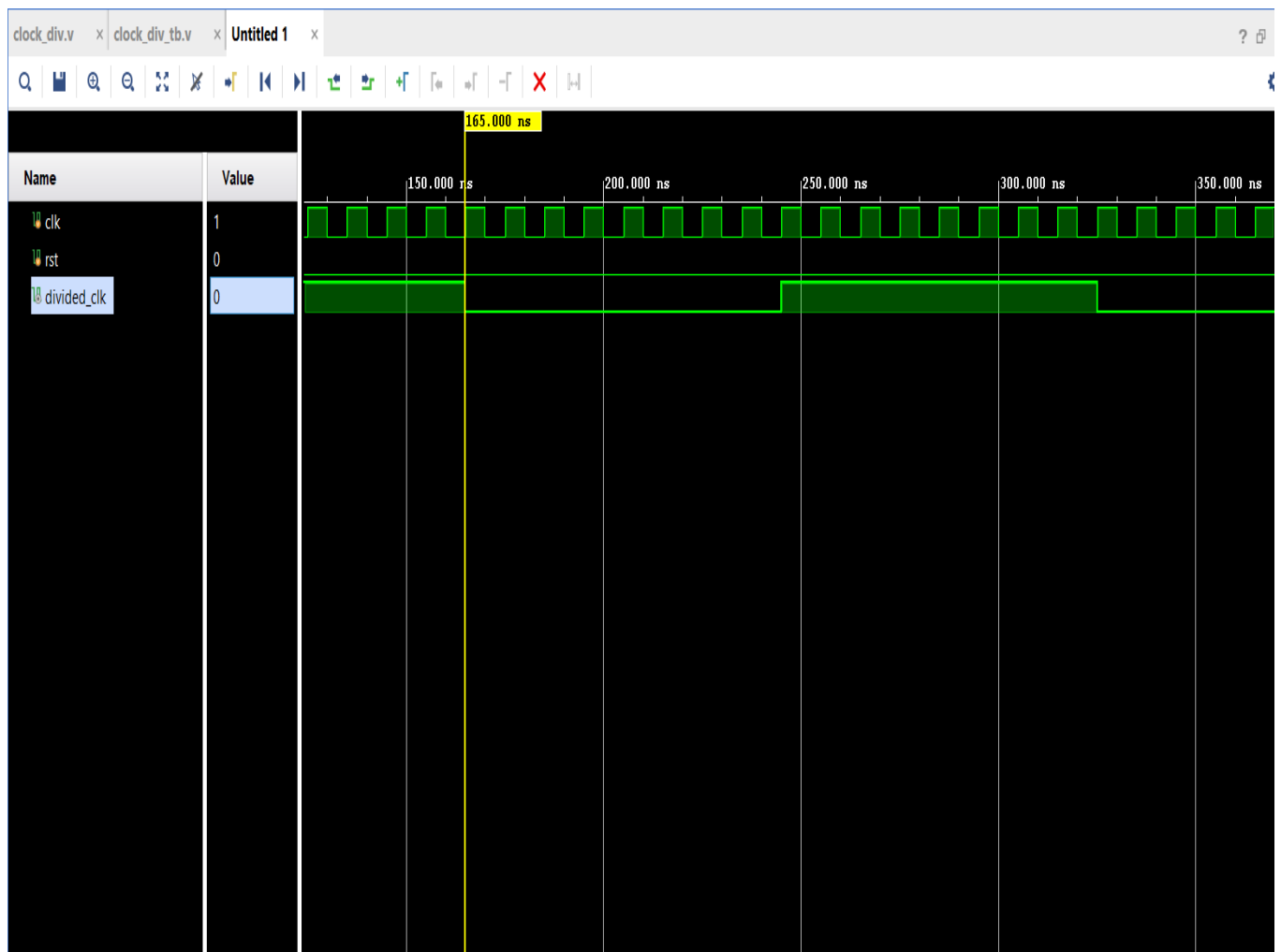


Figure 5 waveforms